




IEEE PELS Workshop on Emerging Technologies: Wireless Power (2018WoW)



Dual-Band Multi-Receiver Wireless Power Transfer with Reactance Steering Network

Ming Liu, Minjie Chen
Princeton University

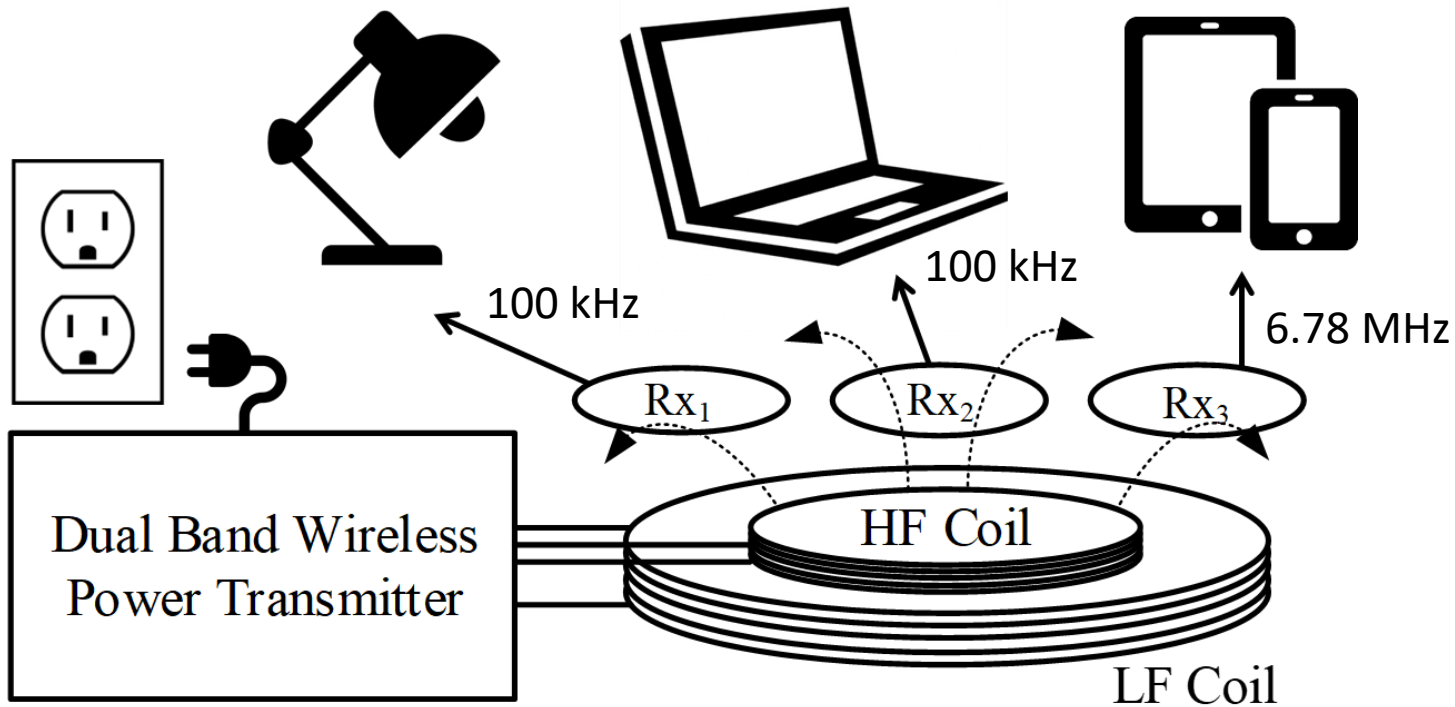Dual-Band Multi-Receiver Wireless Power Transfer



kHz wireless power transfer

- Higher efficiency
- Higher power transfer capability
- Large coil size
- Low tolerant to misalignment


MHz wireless power transfer

- Lower efficiency
- Lower power transfer capability
- Small coil size
- High tolerance to misalignment


Support multiple frequency bands; very wide impedance variation range

Topology Candidates for Dual-Band WPT

Typical kHz WPT Transmitter

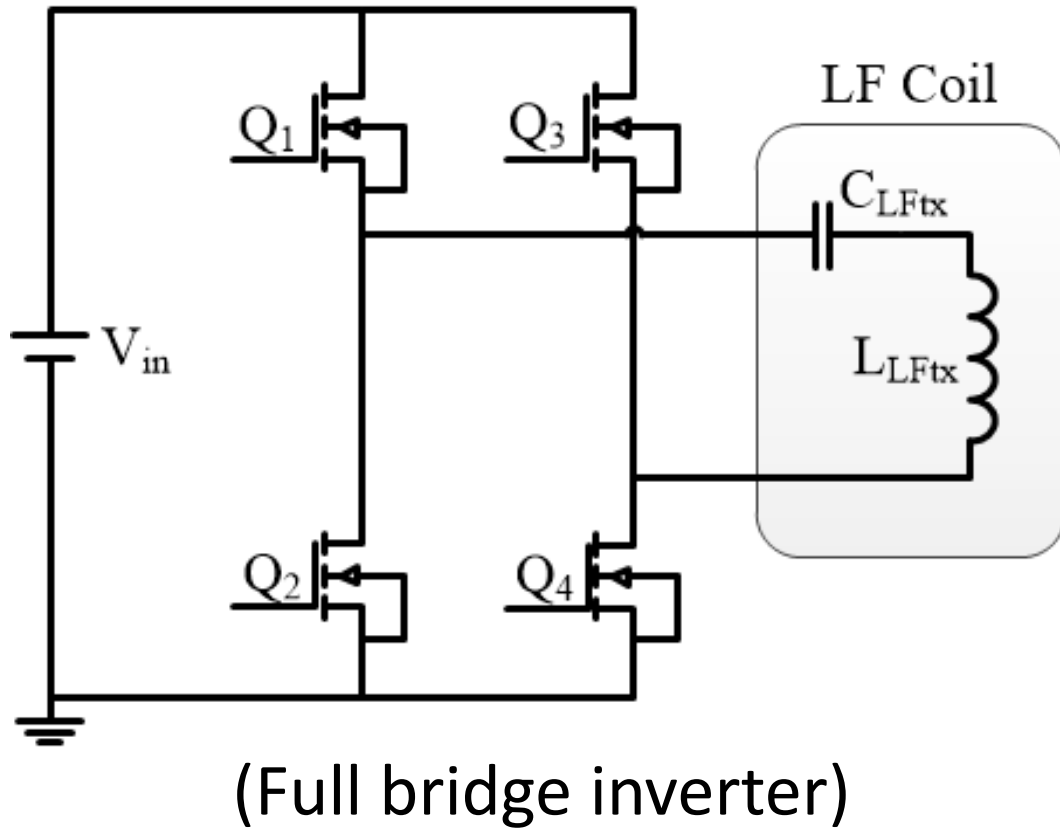


Typical MHz WPT Transmitter

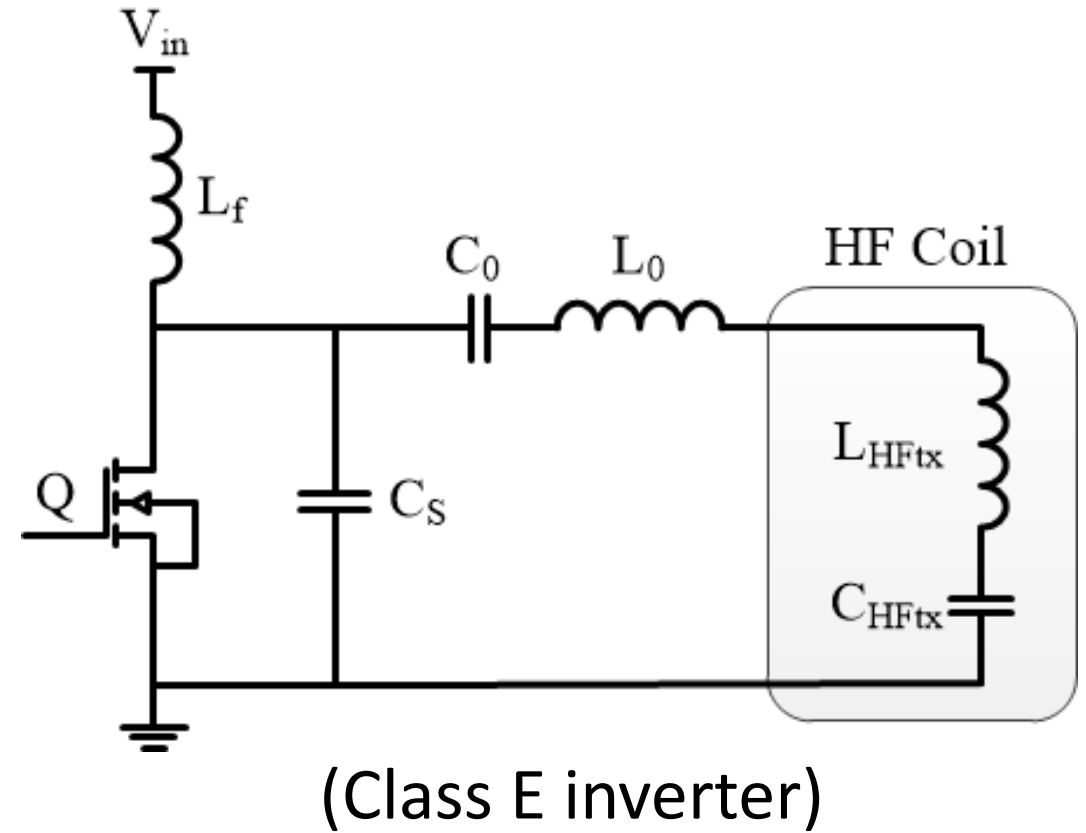


Challenges of HF WPT with Single-Switch PAs

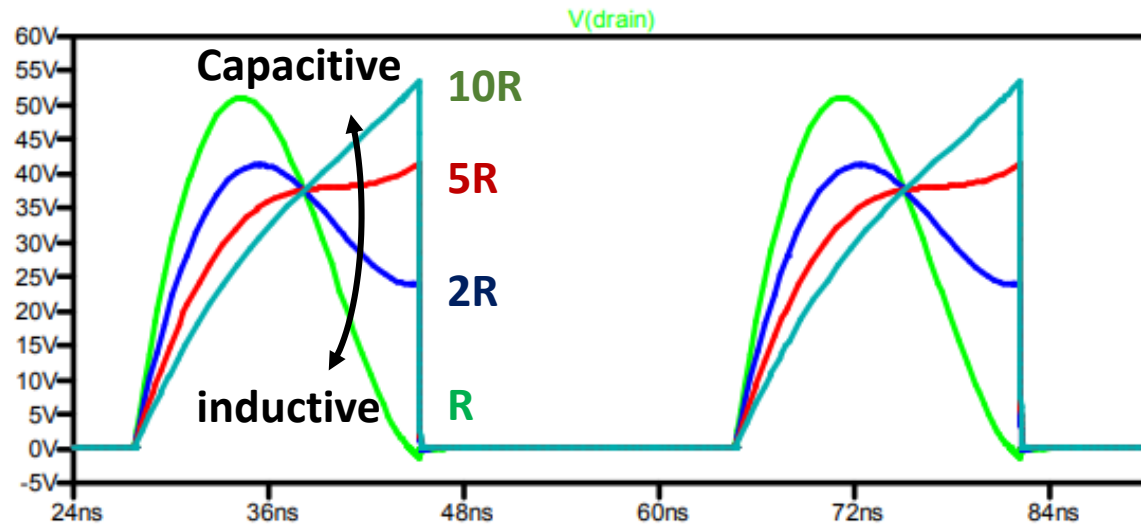- Co-location of multiple receivers induces large impedance variation
- Class-E PAs are sensitive to load impedance variation (resistive and reactive)



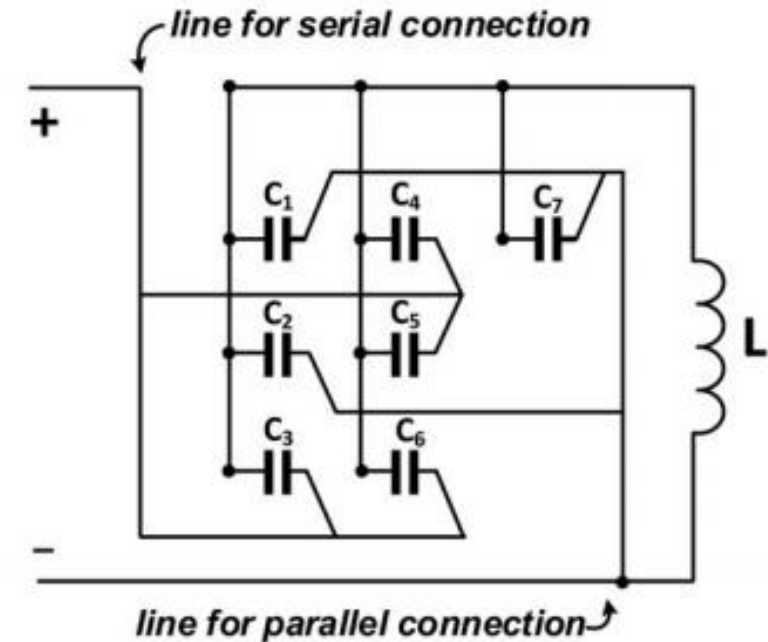
Drain voltage of Class-E PAs with impedance/resistance variation




A switched-capacitor tunable matching network

- N. O. Sokal and A. D. Sokal, "Class E-A new class of high-efficiency tuned single-ended switching power amplifiers," *IEEE Journal of Solid-State Circuits*, vol. 10, no. 3, pp. 168-176, Jun 1975.
- Y. Lim, H. Tang, S. Lim and J. Park, "An Adaptive Impedance-Matching Network Based on a Novel Capacitor Matrix for Wireless Power Transfer," in *IEEE Transactions on Power Electronics*, vol. 29, no. 8, pp. 4403-4413, Aug. 2014.

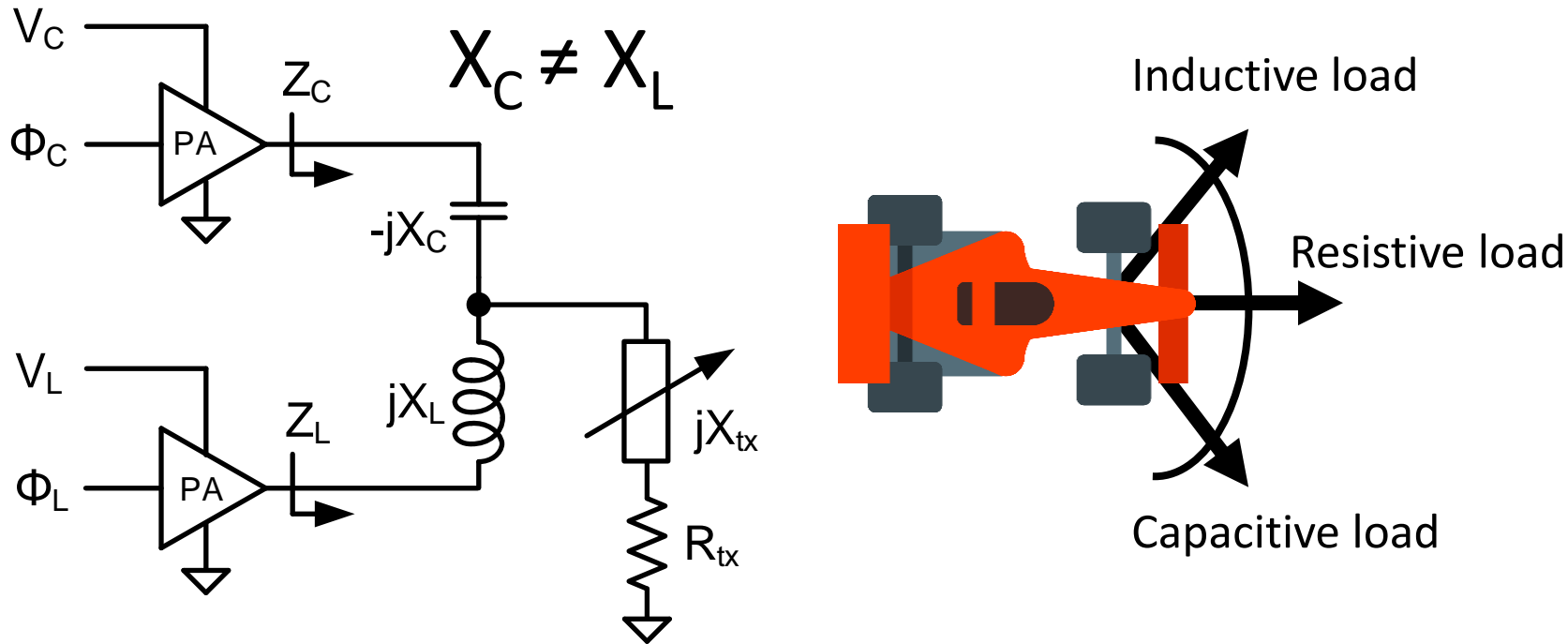
Maintain pure resistive load for both PAs



Inductive load

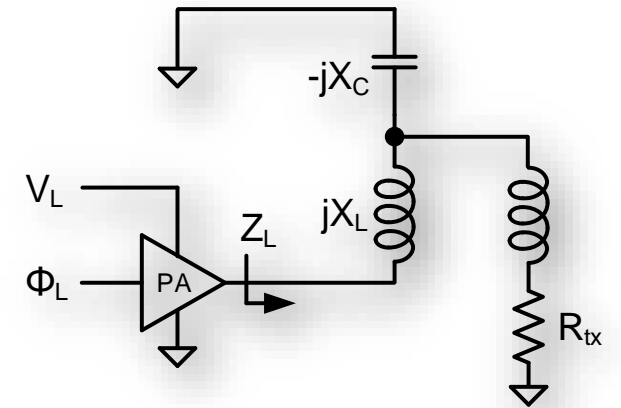


Capacitive load

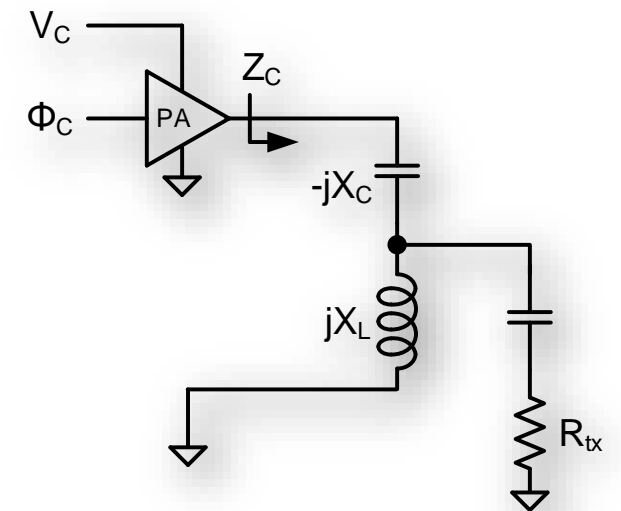


- Steering towards **capacitive** branch with **inductive** load
- Steering towards **inductive** branch with **capacitive** load
- Compensate for large reactance with small X_L and X_C

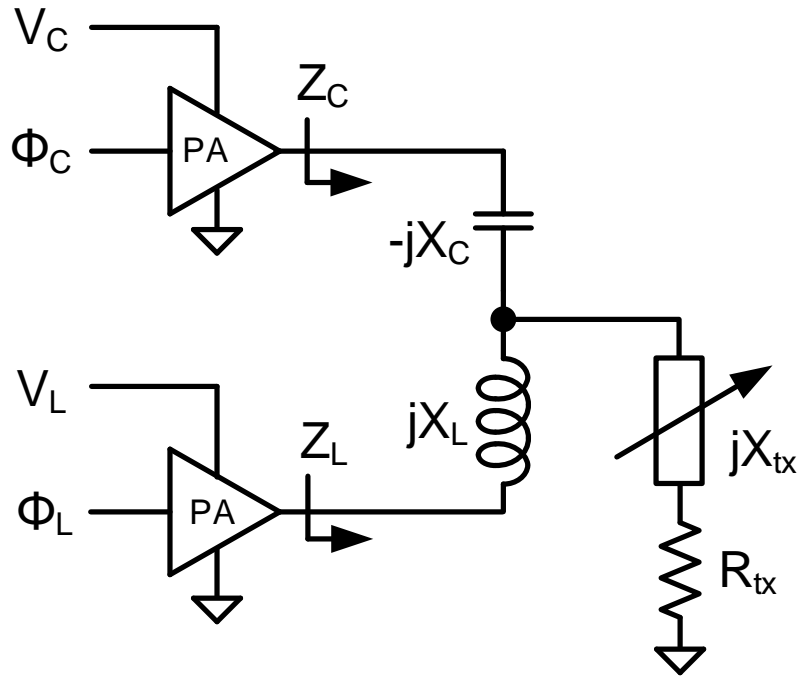
Control of the Reactance Steering Network



Amplitude Ratio

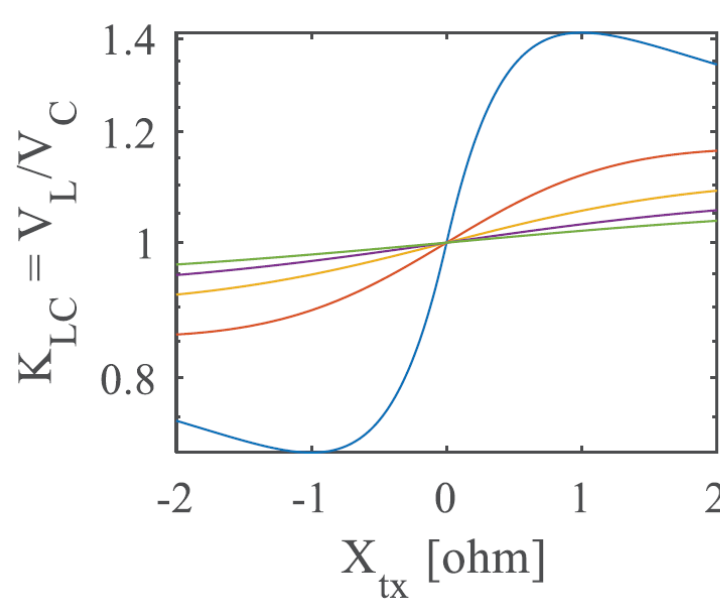

Phase Difference

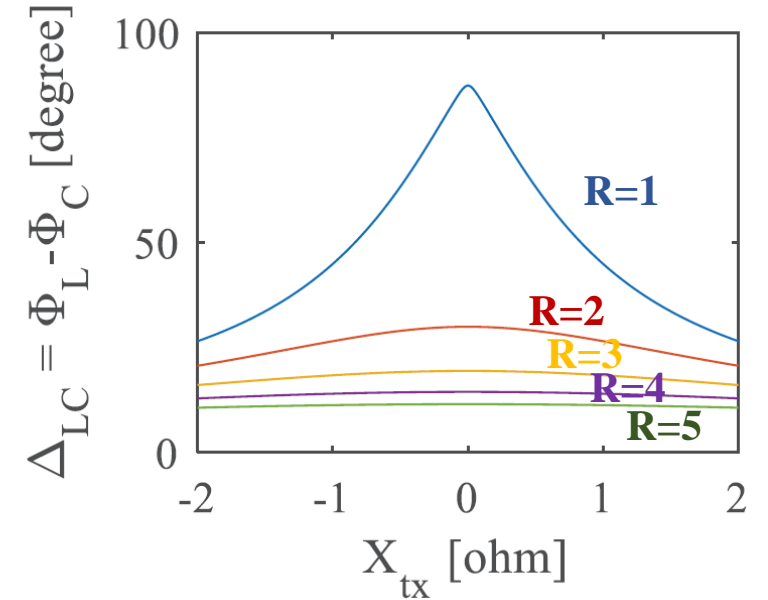

Amplitude Ratio

$$K_{LC} = \left| \frac{V_L}{V_C} \right| = \frac{X_O + X_{tx}}{X_{tx} \cos(\Delta_{LC}) + R_{tx} \sin(\Delta_{LC})}$$






Phase Difference

$$\Delta_{LC} = \Phi_L - \Phi_C = \arcsin \sqrt{\frac{X_O^2}{X_{tx}^2 + R_{tx}^2}}$$

$$\frac{1}{\sqrt{2}} < K_{LC} < \sqrt{2}$$


$$0^\circ < \Delta_{LC} < 90^\circ$$

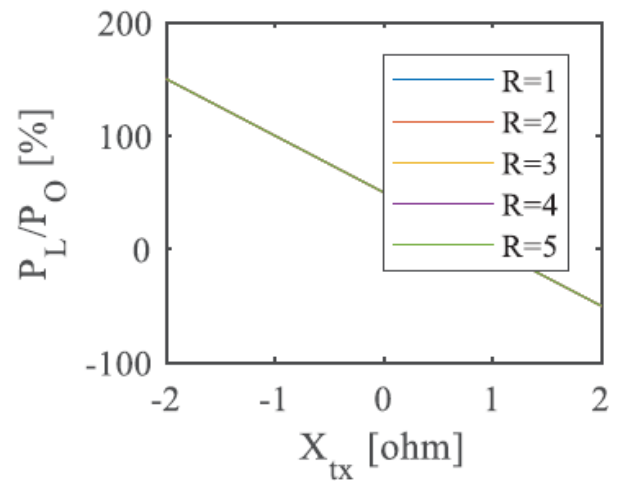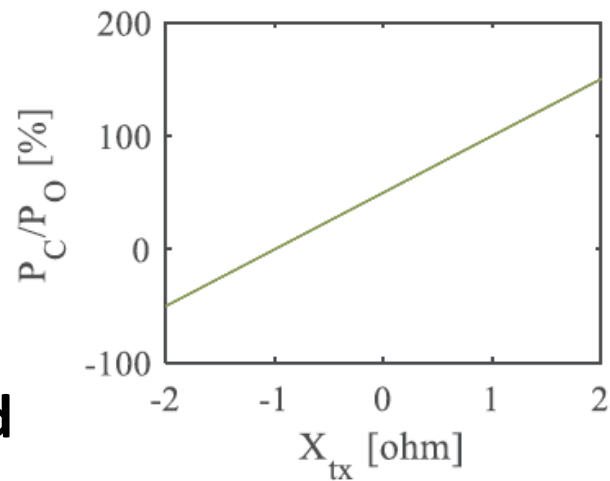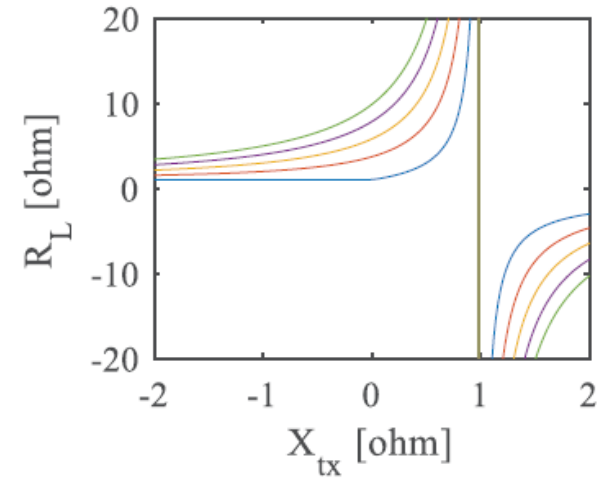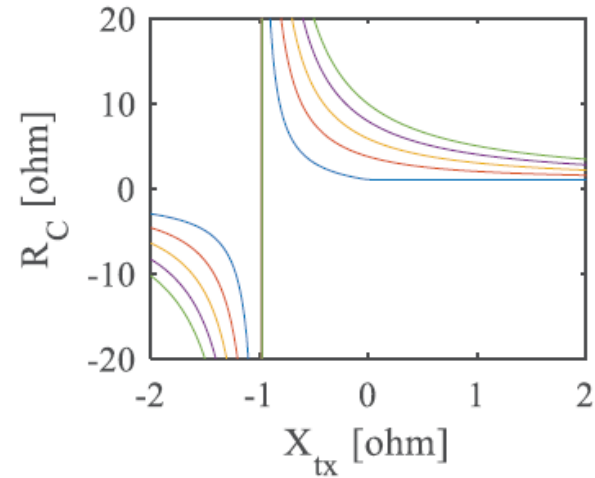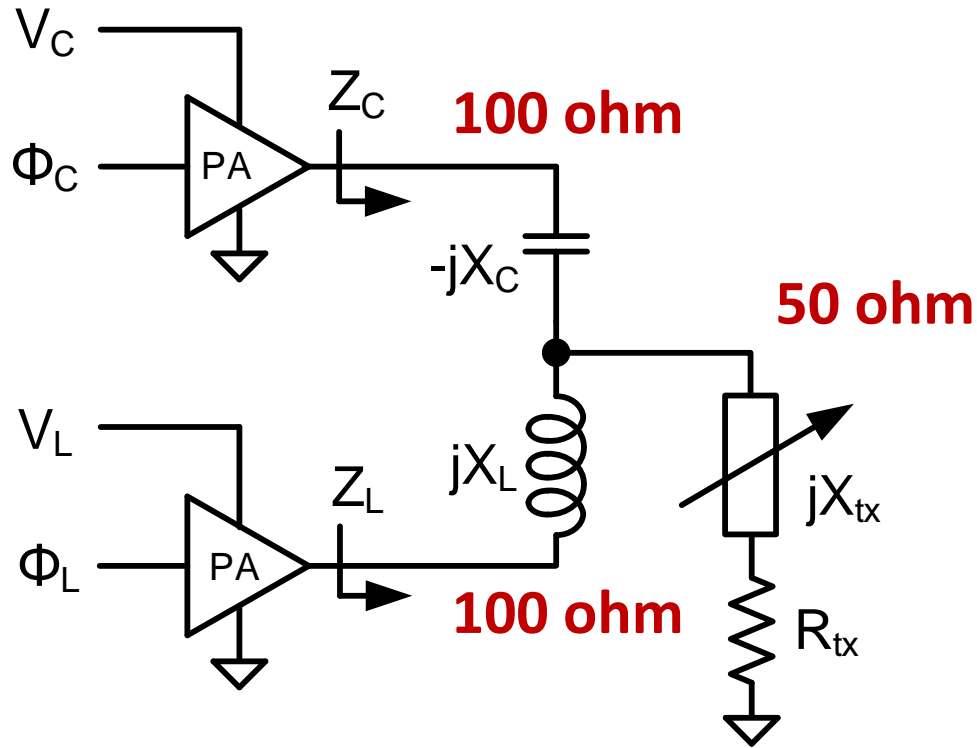Load Resistance and Adaptive Power Sharing




- Both PAs always see pure resistive load
- Both PAs adaptively split the power
- When reactance is very high, one PA functions as a rectifier with negative resistance

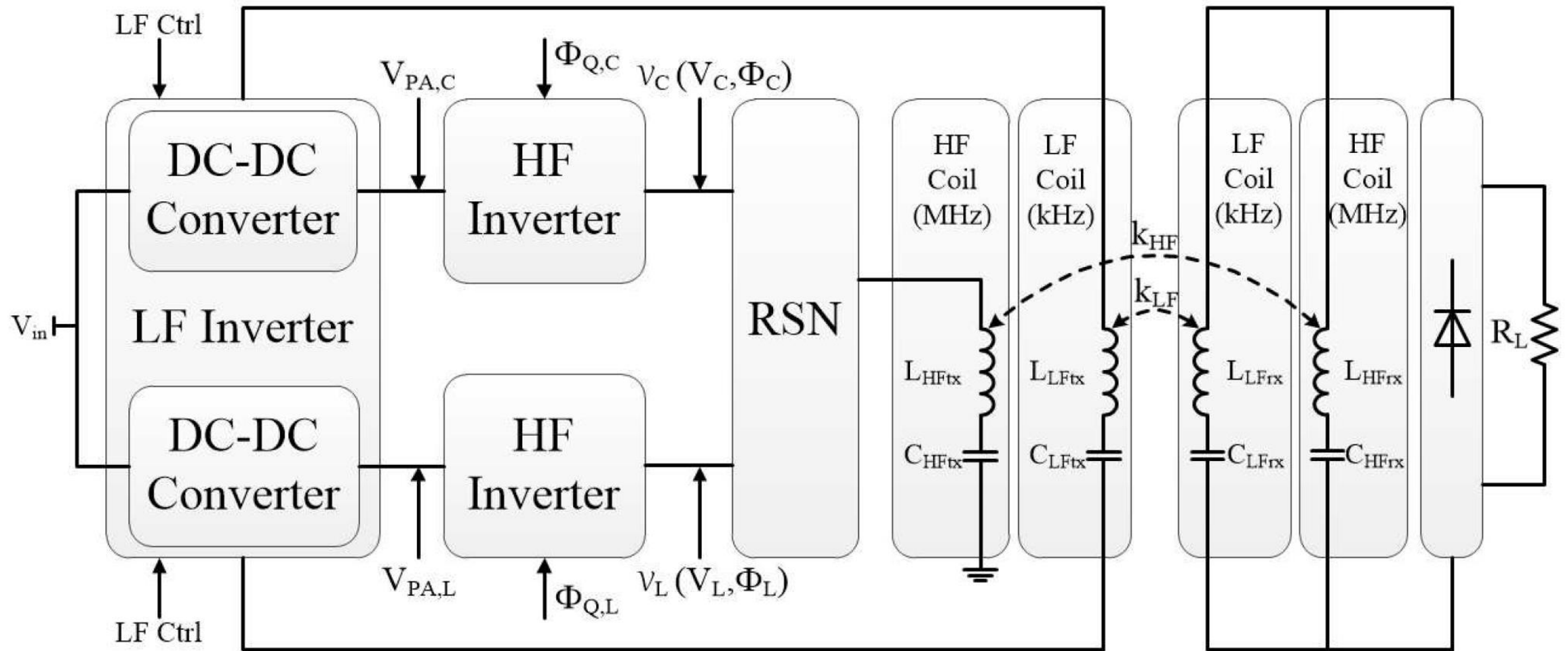Dual-Band Multi-Receiver WPT Architecture with RSN




Merge LF and HF Transmitters, and create mutual advantages

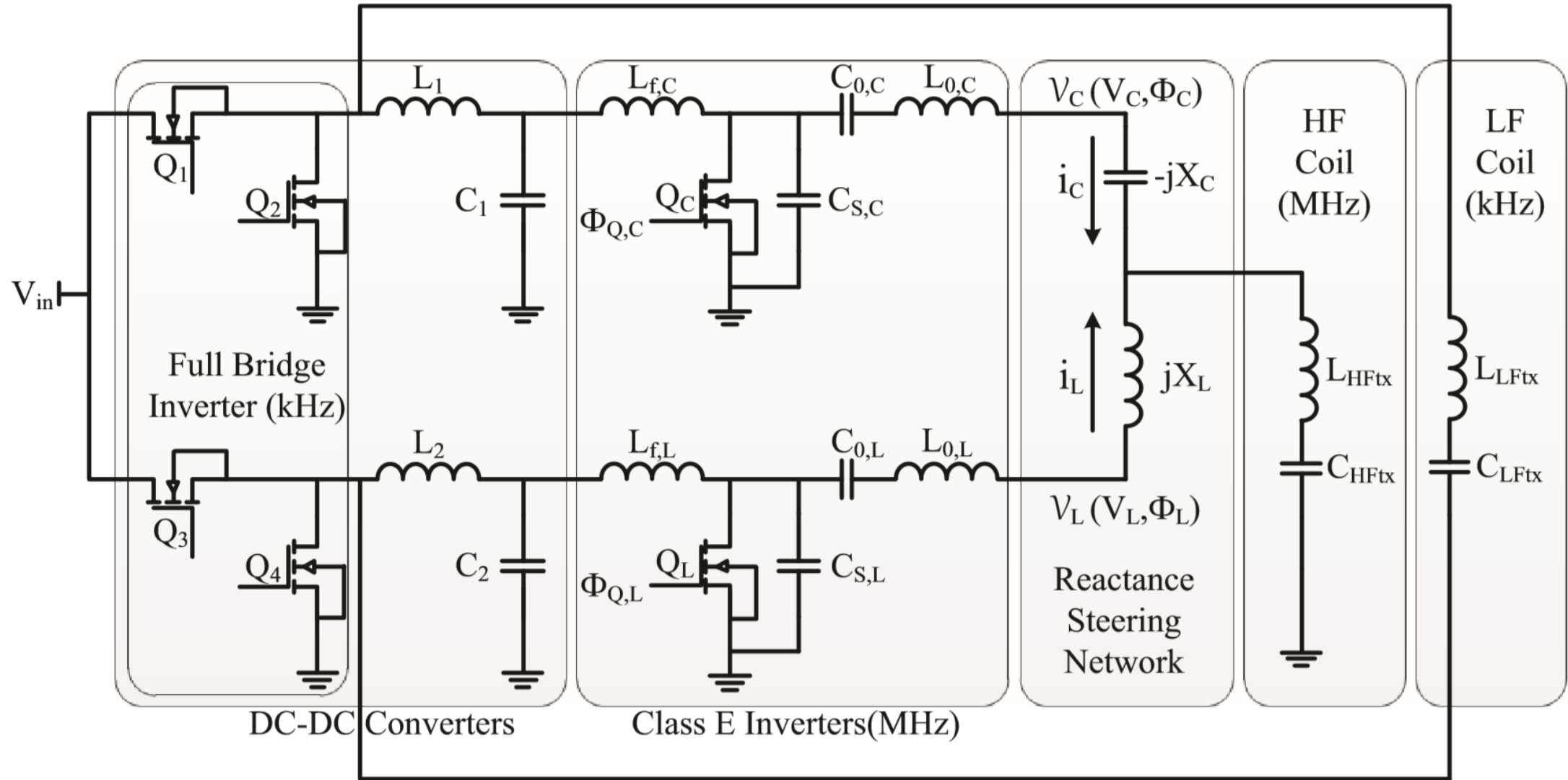Low Component Count Dual Band Transmitter



The dc-dc converters can be implemented as a part of front-end PFC

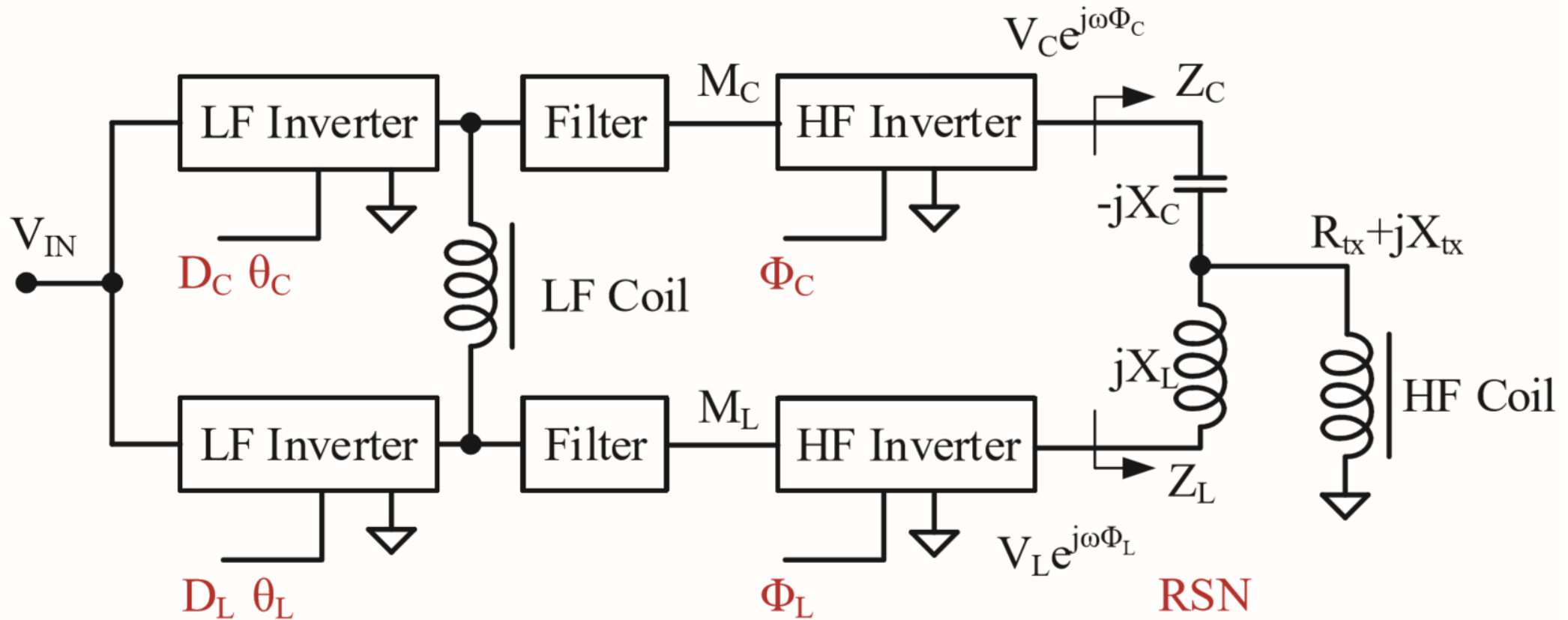Decoupled Control of the HF and LF Operation






Control variables for the HF coil: D_C, D_L, Φ_C, Φ_L


Control variables for the LF coil: $D_C, D_L, \theta_C, \theta_L$

A Dual-Band Multi-Receiver WPT Prototype

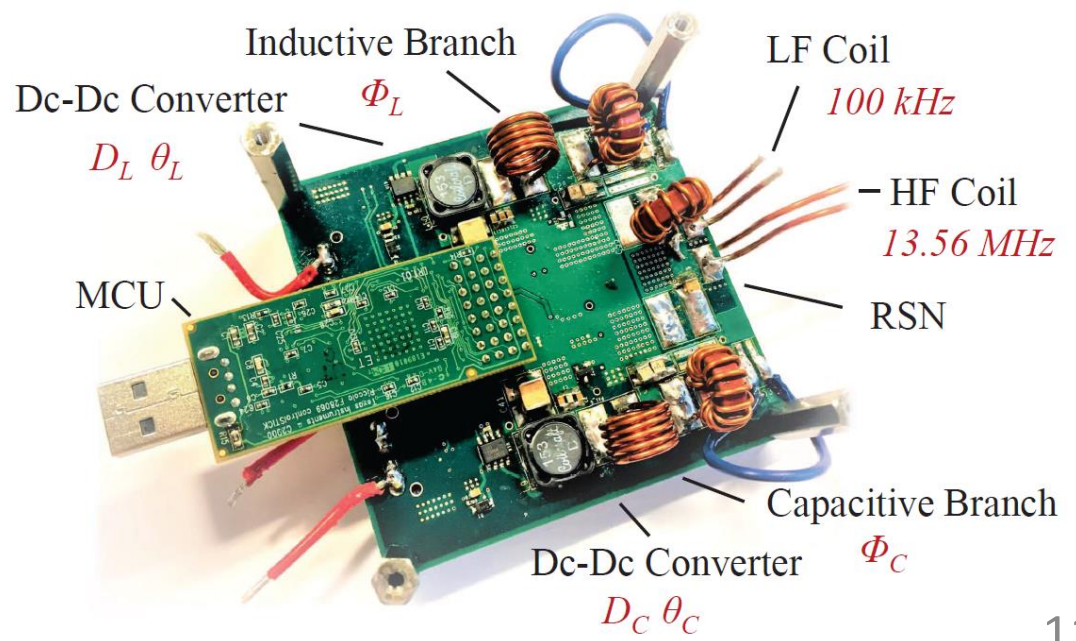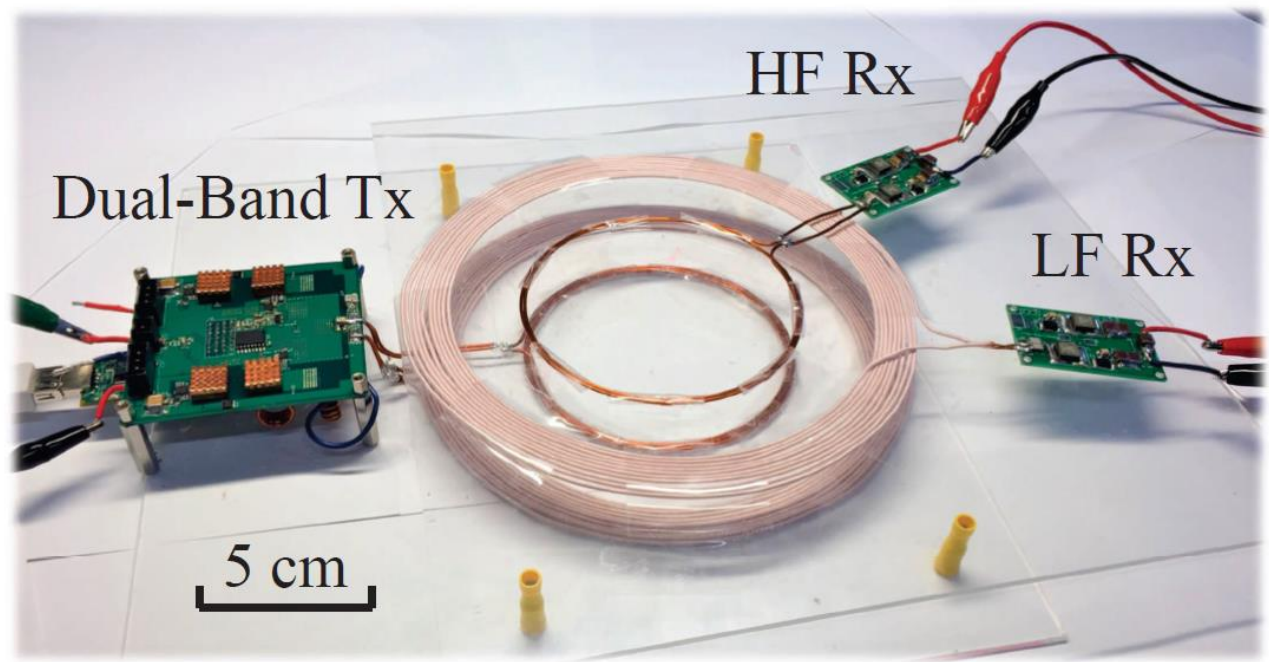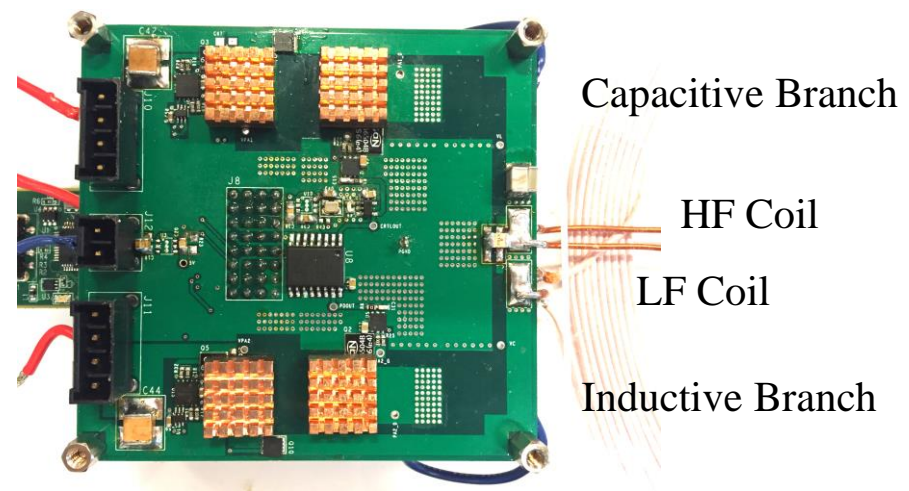
- Dual Band Operation:** 100 kHz and 13.56 MHz
- Power Rating:** 65 W@100 kHz, 65 W@13.56 MHz
- Input Voltage:** 50 V (up to 80 V)
- Output Voltage:** 30 V@100 kHz, 30 V@13.56 MHz
- Spacing:** 2.8 cm distance, up to 3 cm misalignments
- Coil size:** Coil_HF (D=10 cm), Coil_LF (D=20 cm)



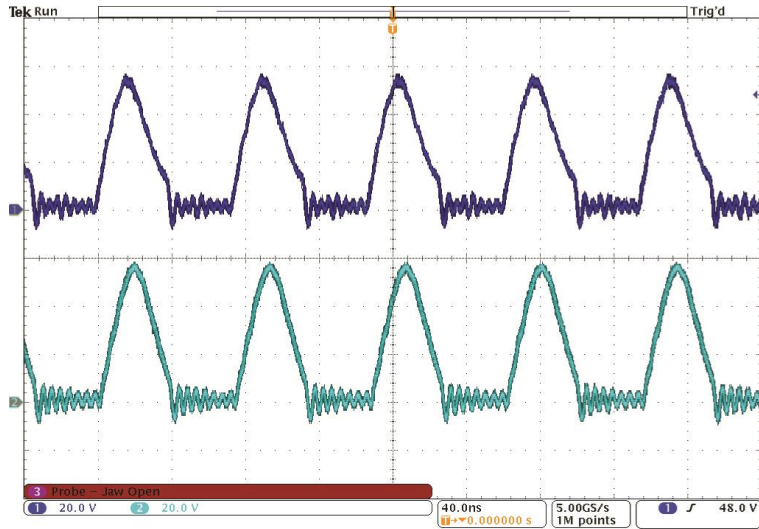ZVS of Both Class-E PAs across Very Wide Reactance Range




Example drain voltage without RSN

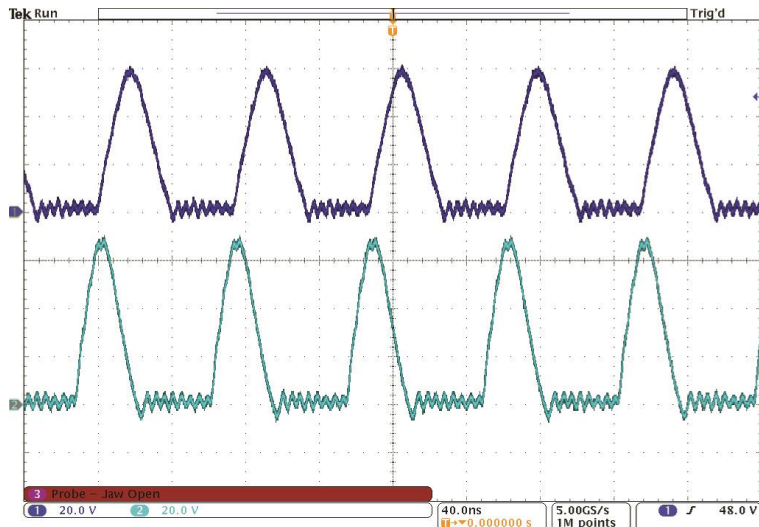

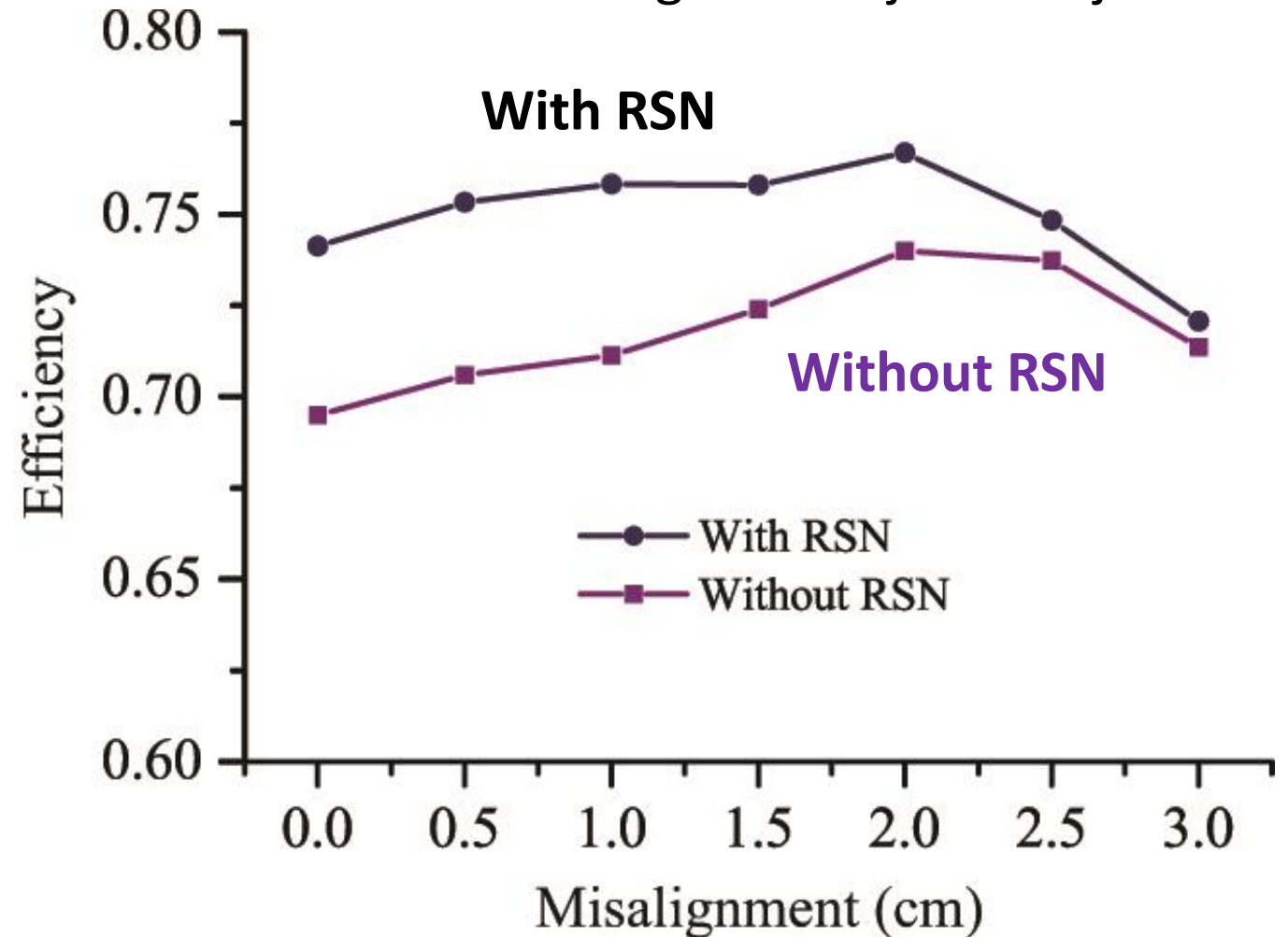
Example drain voltage with RSN

- Efficiency vs. misalignment (0 ~ 3 cm)
- Fixed output power 30W
- Reactance range from $0j \Omega$ to $80j \Omega$




Decoupled Modulation of the Two Bands

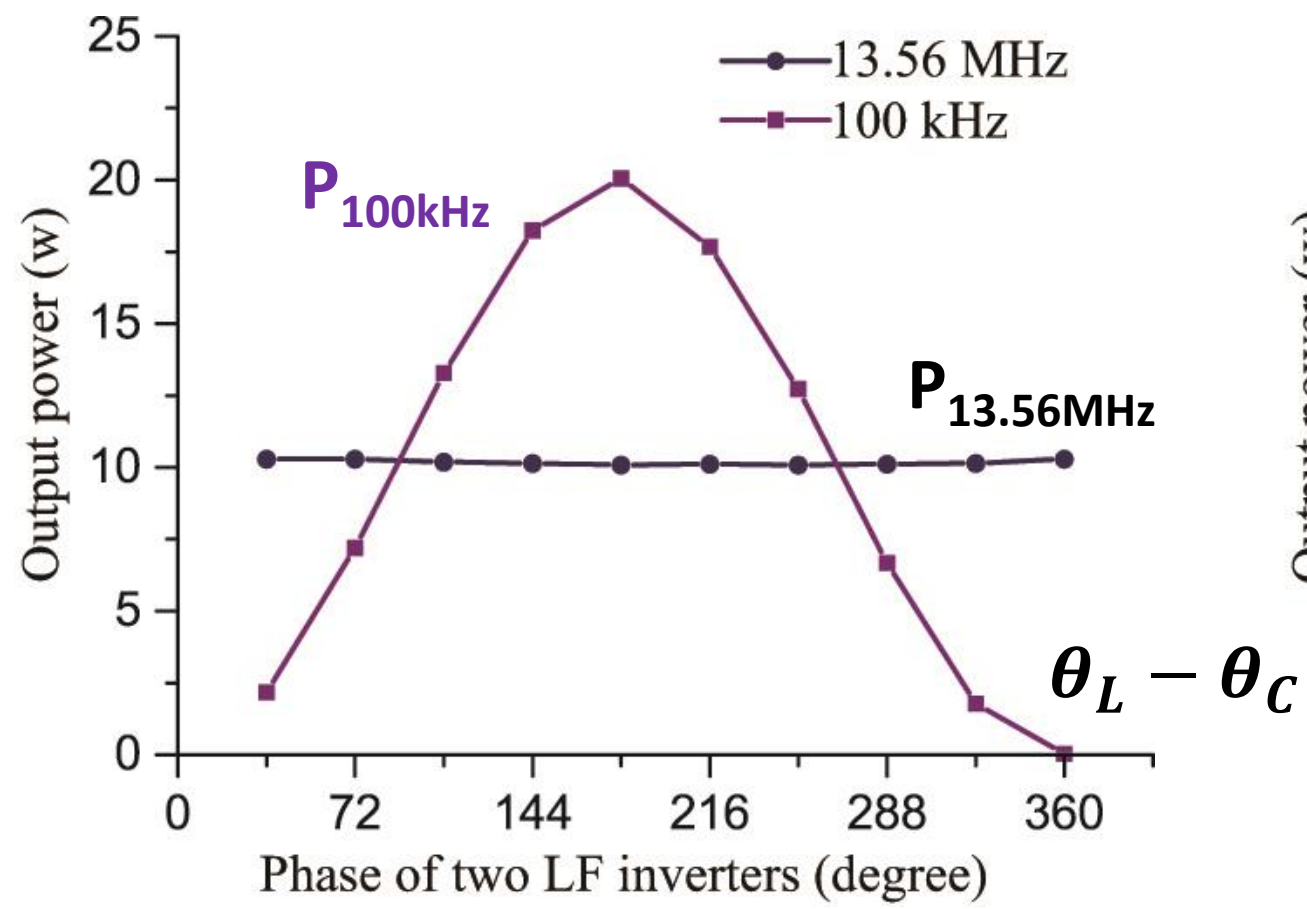- Modulating power at 100 kHz
- Maintaining 10 W at 13.56 MHz



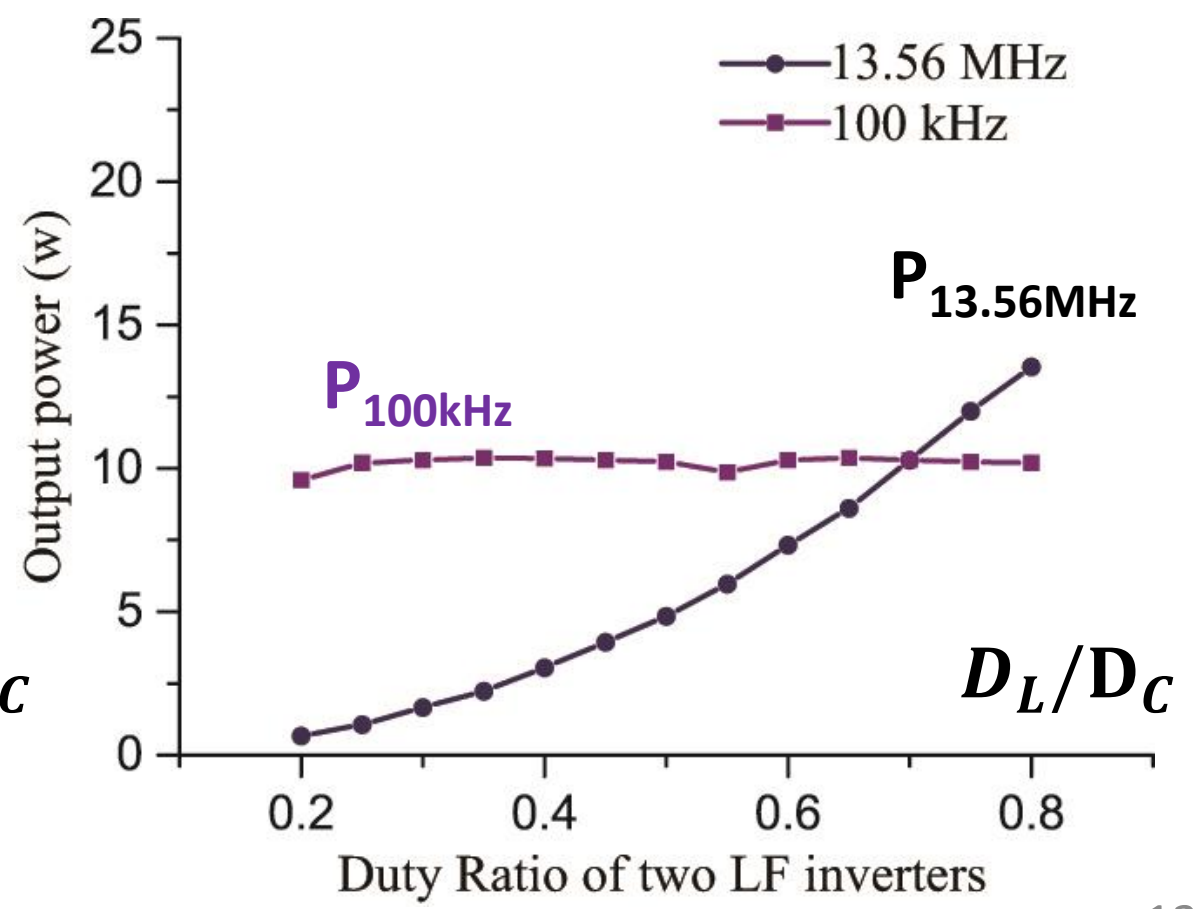
- Modulating power at 13.56 MHz
- Maintaining 10 W at 100 kHz



HF WPT Efficiency with “Very” Reactive Load


- RSN significantly improves the HF WPT efficiency with capacitive X_{tx} .
- RSN sacrifices more loss with very inductive load (due to circulating current).

R: 50 Ω
X: -200 Ω to +200 Ω

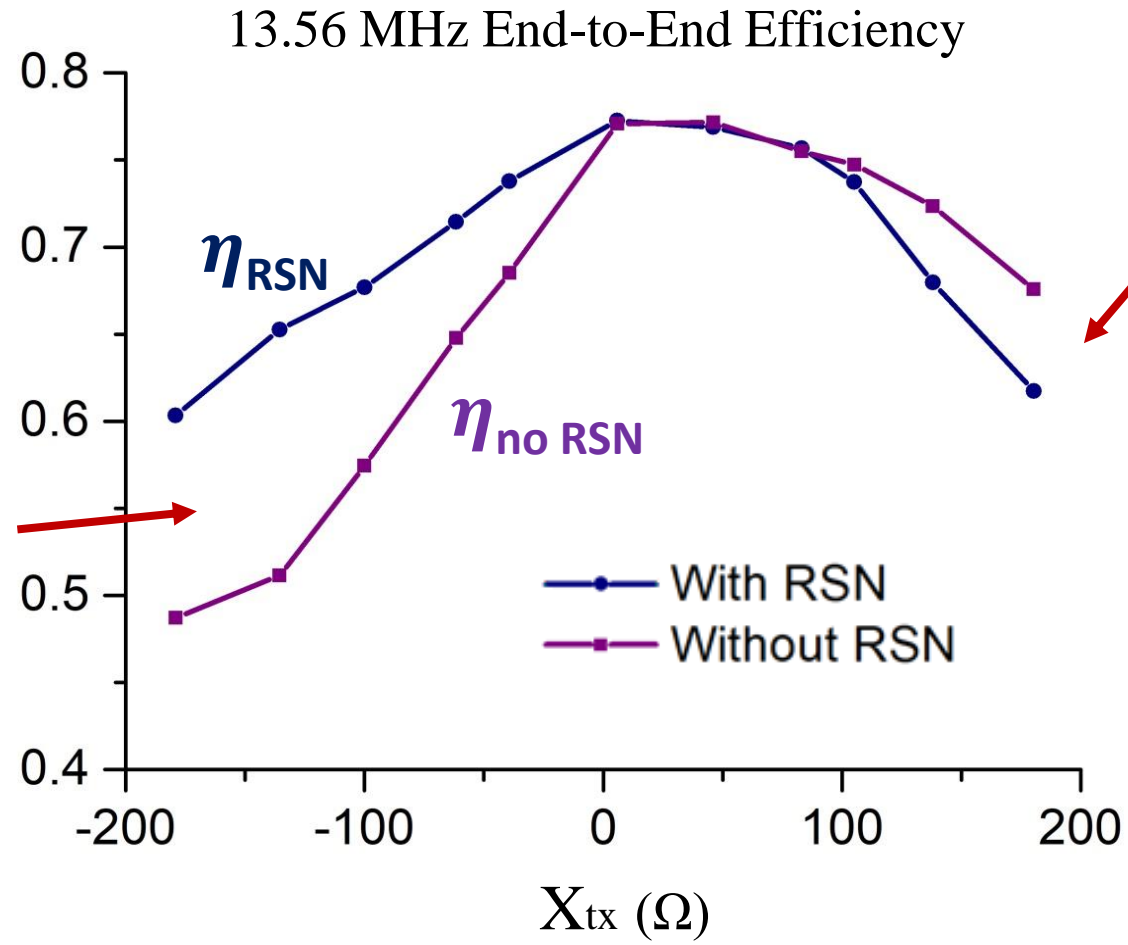

12% higher efficiency with “very” capacitive load


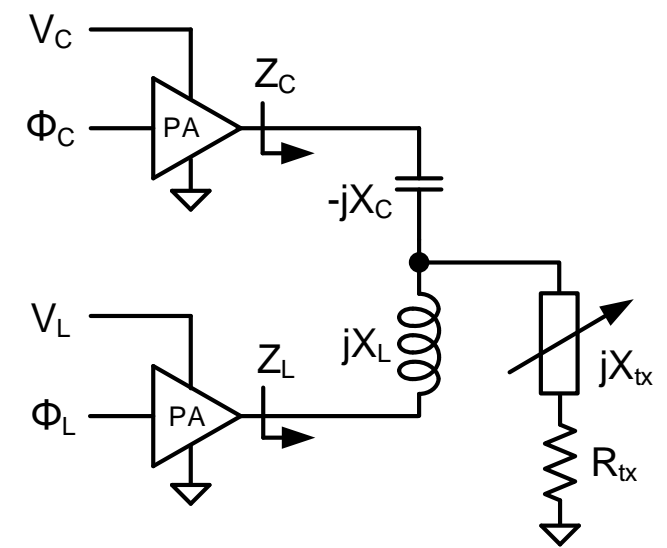
4% lower efficiency with “very” inductive load



Demo: A Dual-band Wireless Powered Desktop System



**Demo: a dual-band wireless
powered desktop computer**

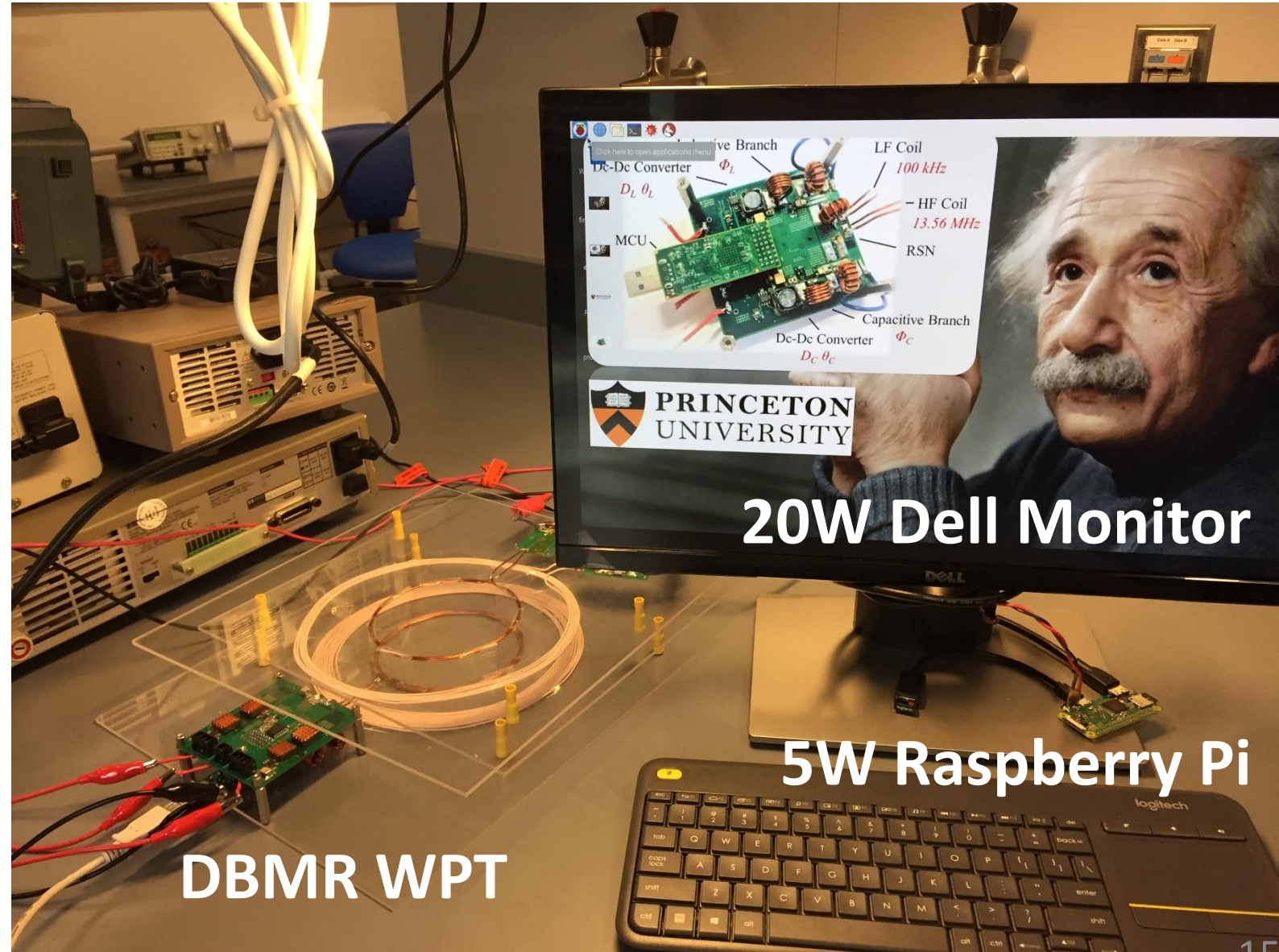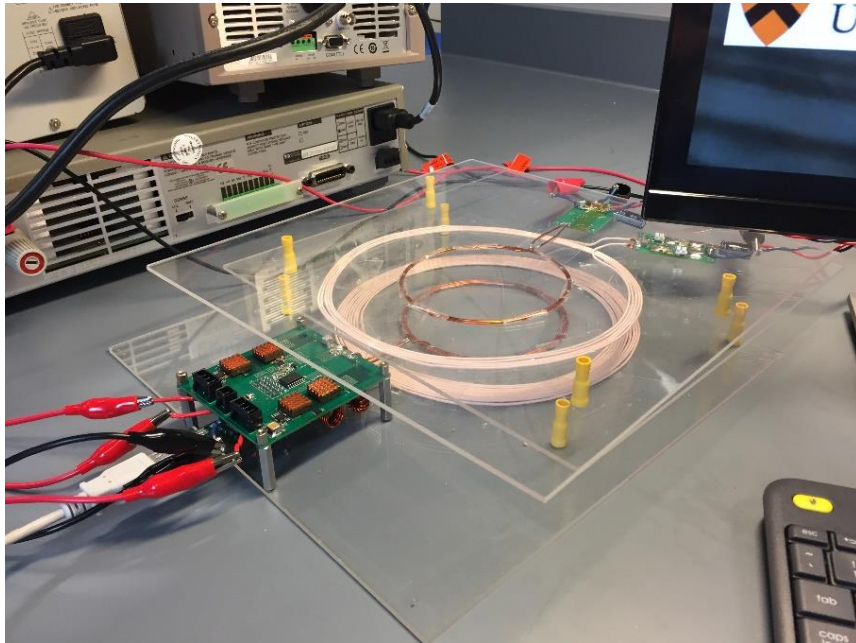Dell Monitor: 20W @ 100 kHz
Raspberry Pi: 5W @ 13.56 MHz
Efficiency: ~ 75%, end to end



Summary

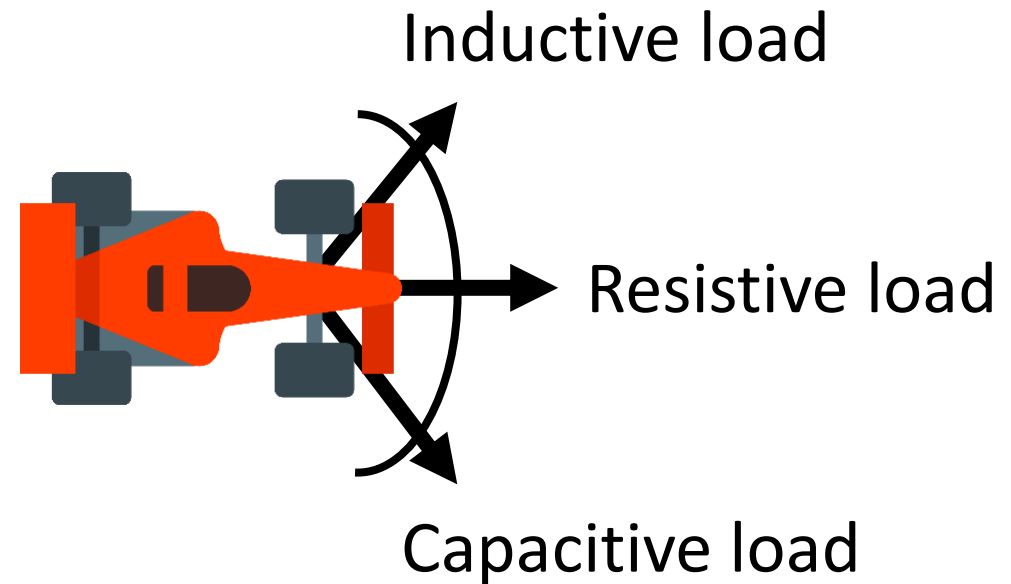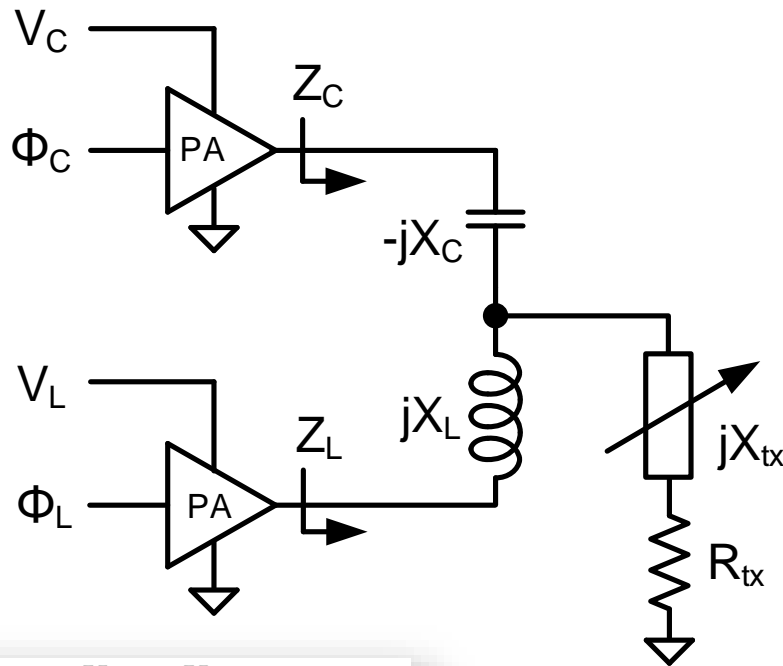- Theory: Reactance Steering Network (RSN) for RFPAs.
- Application: HF/VHF power conversion with load impedance variation.
- Example: A dual-band multi-receiver wireless power transfer system.



$$K_{LC} = \left| \frac{V_L}{V_C} \right| = \frac{X_O + X_{tx}}{X_{tx} \cos(\Delta_{LC}) + R_{tx} \sin(\Delta_{LC})}$$

$$\Delta_{LC} = \Phi_L - \Phi_C = \arcsin \sqrt{\frac{X_O^2}{X_{tx}^2 + R_{tx}^2}}$$

Fully active load impedance compensation